

---


### Problem Statement:

- (a) Write a Verilog module to implement a 2-to-1 multiplexer (MUX) at (i) structural level using elementary two-input logic gates (NOT, NAND, NOR), (ii) behavioural level. Using this module and other elementary two-input logic gates as necessary, build a 2<sup>n</sup>-to-1 MUX that can implement any Boolean function of 5 variables.
- (b) Write a Verilog module to implement a clock-enabled JK flip-flop (Jack Kilby flipflop) at (i) structural level using elementary two-input logic gates (NOT, NAND, NOR), (ii) behavioural level. Using this module and other two-input logic gates as necessary, build a four-bit synchronous binary counter.

### Solution:

(a) Verilog Module for 2-to-1 multiplexer (MUX)

i. Structural Level:

 

Equation from the circuit:  $Y = D0.S' + D1.S$

- **Module:**

```

module m1(Y, D0, D1, s);
output Y;
input D0, D1, s;
wire T1, T2, s1;           // Defining Intermediate outputs and inputs
nand n1(s1,s,s);           // s1 is the compliment of s. s1=~s
nand u1(T1, D0, s1);
nand u2(T2, D1, s);
nand u3(Y, T1, T2);
endmodule

```

- Test Bench module:

```

`include "stru21.v"
module mux_tst;
// Inputs
reg D0;
reg D1;
reg s;
//output
wire Y;

//Instantiate the unit under test
m1 uut (.Y(Y), .D0(D0), .D1(D1), .s(s));


initial
begin
$dumpfile("backend.vcd"); $dumpvars(0,mux_tst);
end

initial begin
//initialise inputs
D0=0;
D1=0;
s = 0;
end
always #2 s=s+1;
always #1 D0=D0+1;
always #5 D1=D1+1;
initial #20 $finish;

endmodule

```

- Waveforms:

 

## ii. Behavioural Level:

Truth Table:

Select line	Input		Output
S	D0	D1	Y
0	0	0	0
0	0	1	1
1	1	0	1
1	1	1	1

Equation from the truth table:  $Y = D0.S' + D1.S$

## • Module:

---

```
module m21( D0, D1, s, Y);  
input  D0, D1, s; //Defining inputs  
output reg Y;     // Defining output  
  
always @(D0 or D1 or s)  
begin  
  
    if(s)  
        Y= D1;           //if s=1 then Y= D1  
    else  
        Y=D0;           //if s=0 then Y= D0  
  
end  
  
endmodule
```

- Test Bench:

```

`include "2_11.v"
module mux_tst;
// Inputs
reg [1:0] in;
reg s;

//output
wire out;

//Instantiate the unit under test
m1 uut (in[0],in[1],s,out);


initial
begin
$dumpfile("backend.vcd"); $dumpvars(0,mux_tst);
end

initial begin
//initialise inputs
in=2'b0;
s = 0;
end
always #2 s=s+1;
always #1 in=in+1;
initial #20 $finish;

endmodule


```

- Waveform:

 

(b) Verilog module to implement a clock-enabled JK flip-flop:

- Structural Level:

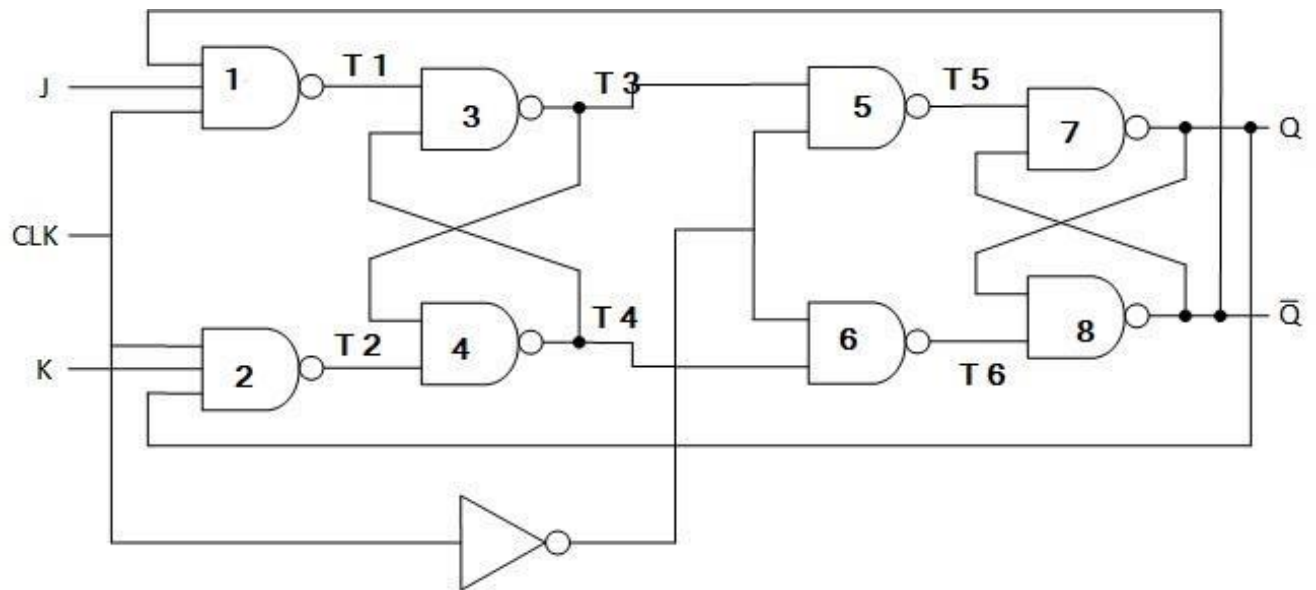

- **Module:**

```

module jk11 (Q,Q_bar, J, K, clk);
output Q, Q_bar; //outputs
input J, K, clk; //inputs
wire T1, T2, T3, T4, T5, T6; //Intermediate states
initial
begin
wire Q=1'b0;
wire Q_bar=1'b1;
end
// Implementation of JK flip flop using Nand gate
nand u1 (T1, J, Q_bar, clk);
nand u2 (T2, K, Q, clk);
nand u3 (T3, T1, T4);
nand u4 (T4, T2, T3);
nand u5 (T5, T3, ~clk);
nand u6 (T6, T4, ~clk);
nand u7 (Q, T5, Q_bar);
nand u8 (Q_bar, T6, Q);

endmodule

```

- 


## Test Bench

```
`include "2222.v"
module tb_JK();
// Inputs
reg J;
reg K;
wire Q;
reg clk=0;

always #5 clk=~clk ;
//Instantiation
jkl1 st (.J(J), .K(K), .clk(clk), .Q(Q), .Q_bar(Q_bar));
initial
begin
  $dumpfile("backend.vcd"); $dumpvars(0,tb_JK);
end

 initial begin
  J=0 ;
  K=0 ;
  #20
  J=0 ;
  K=1 ;
  #20
  J=1 ;
  K=0 ;
  #20
  J=1 ;
  K=1 ;
  #20 $finish;
end
endmodule
```






 

 
 
- Waveform:





ii. Behavioural Level:

Truth Table:

Trigger	Inputs		Output				Inference
			Present State		Next State		
CLK	J	K	Q	Q'	Q	Q'	
	x	x	-		-		Latched
	0	0	0	1	0	1	No Change
			1	0	1	0	
	0	1	0	1	0	1	Reset
			1	0	0	1	
	1	0	0	1	1	0	Set
			1	0	1	0	
	1	1	0	1	1	0	Toggles
			1	0	0	1	

• Module:

```

module JK_FF(
    // Inputs
    input J,
    input K,
    input clk,
    // Outputs
    output Q,
    output Q_bar
);
    reg Q=0; // Initialization
    always@(posedge clk)
    case ({J,K})
        2'b00: Q<=Q;
        2'b01: Q<=0;
        2'b10: Q<=1;
        2'b11: Q<=~Q;
    endcase
end

initial
begin
    $dumpfile("backend.vcd"); $dumpvars(0,JK_FF);
end

assign Q_bar=~Q;
endmodule

```



- 

### Test Bench:

```
`include "final_jk_behavioural.v"


module tb_JK();
// Inputs
reg J;
reg K;
// Outputs
wire Q;
wire Q_bar;
reg clk=0;    // Clock Initialization
always #5 clk=~clk; // In every 5 second clock changes its state.

//Instantiate
JK_FF st (.J(J), .K(K), .clk(clk), .Q(Q), .Q_bar(Q_bar));


initial
begin
$dumpfile("backend.vcd"); $dumpvars(0,tb_JK);
end

initial begin
J=0 ;
K=0 ;
#20
J=0 ;
K=1 ;
#20
J=1 ;
K=0 ;
#20
J=1 ;
K=1 ;
#20 $finish;
end
endmodule
```

- Waveforms:

 
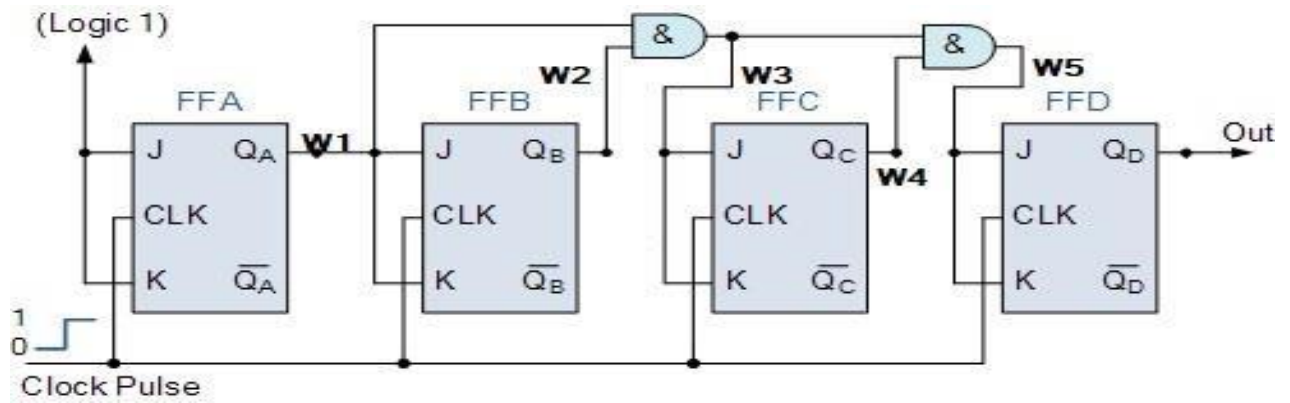
### iii. 4 bit Synchronous Counter using JK Flip Flop:



- Module:

```

module jk_ff ( j, k, clk, q);
//inputs
input j;
input k;
input clk;
output q;
reg q = 0; // Initialization

//Module of JK FF
always @ (posedge clk)
case ({j,k})
2'b00 : q <= q;
2'b01 : q <= 0;
2'b10 : q <= 1;
2'b11 : q <= ~q;
endcase
endmodule

// Module of Counter
module four_bit_jk(j,k,clk,q,c);
input j,k,clk;
output q;
output [3:0]c;
wire w1,w2,w3,w4,w5;
/*always
begin
w3=w1&w2;
w5=w3&w4;
c={w1,w2,w4,q};*/
assign w3=w1&w2;
assign w5=w3&w4;
jk_ff j1 (j,k,clk,w1);
jk_ff j2 (w1,w1,clk,w2);
//and a1 (w3,w1,w2);
jk_ff j3 (w3,w3,clk,w4);
//and a2 (w5,w3,w4);
jk_ff j4 (w5,w5,clk,q);
assign c={q,w4,w2,w1};
endmodule

```

Test Bench:

```

module four_bit_jk_tb;
    reg j;
    reg k;
    reg clk;
    wire q;
    wire [3:0]c;

    always #5 clk <= ~clk;
    //Instantiation
    four_bit_jk    jk0 ( .j(j),
                        .k(k),
                        .clk(clk),
                        .q(q),.c(c));

    // Initialization
    initial begin
        clk<=0;
        j <= 1;
        k <= 1;

        #2000 $finish;
    end

    initial
    begin
        $dumpfile("backend.vcd");
        $dumpvars(0,four_bit_jk_tb);
    end

endmodule

```

- Waveform:



